
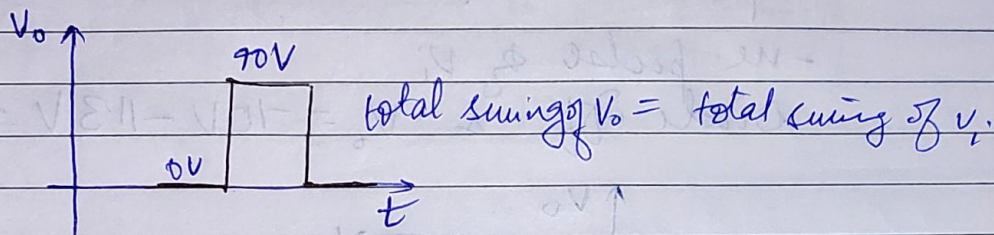


Tutorial - 3

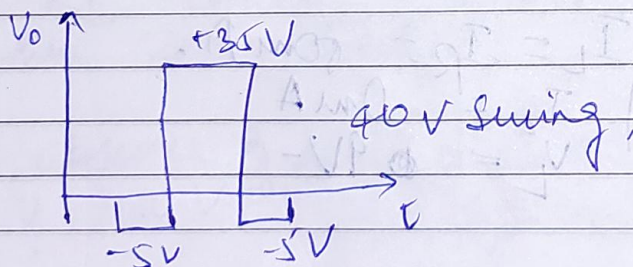- 1(a) starting w/ $V_i = -20V$ the diode is in the 'on' state & capacitor quickly charges to $20V$. During this interval of time V_o is across the on diode (short-circuit eqv) & $V_o = 0$.
 when V_i switches to the $+20V$ level, diode goes to 'off' state (open-circuit) &
 $V_o = V_i + V_c = 20 + 20 = 40V$.



- (b) starting w/ $V_i = -20V$, the diode is 'on' & capacitor quickly charges up to $-15V$.
 $V_i = +20V$ & $5V$ supply are additive across the capacitor. During this time interval V_o is across 'on' diode & $5V$ supply & $V_o = -5V$.
 when V_i switches to the $+20V$ level the diode becomes 'off' & $V_o = V_i + V_c = 25V$.




3 a) $\tau = RC = 5.6 \text{ ms}$
 $\tau_2 = 28 \text{ ms}$

(b) $\tau_2 = 28 \text{ ms} \Rightarrow \frac{T}{2} = \frac{1}{2} = 0.5 \text{ ms} \Rightarrow 56:1$

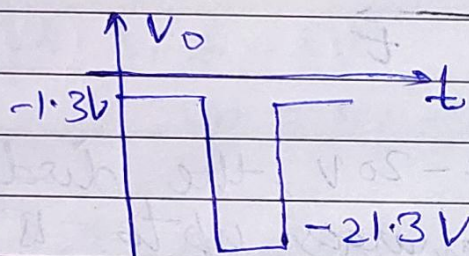(c) the pulse of V_i
 Diode on $V_o = -1.3 \text{ V}$
 capacitor charges to $10 + 2 - 0.7 = 11.3 \text{ V}$

-ve pulse of V_i

Diode off $V_o = -10 \text{ V} - 11.3 \text{ V} = -21.3 \text{ V}$



Q. (a) In the absence of Zener diode

$V_L = 9 \text{ V} < V_Z = 10 \text{ V}$ & diode non conducting

$I_L = I_R = 50 \text{ mA}$
 w/ $I_Z = 0 \text{ mA}$
 $V_L = 9 \text{ V}$

(b) In the absence of Zener diode
 $V_L = 13.62 \text{ V}$.

$\Rightarrow V_L > V_Z$, Zener diode on

$$\therefore V_Z = 10 \text{ V}, V_R = 10 \text{ V}$$

$$I_{R_s} = V_{R_s} / R_s = 10 / 220 = 45.45 \text{ mA}$$

$$I_L = V_L / R_L = 10 / 470 = 21.28 \text{ mA}$$

$$I_Z = I_{R_s} - I_L = 24.17 \text{ mA}$$

$$(c) P_Z = 400 \text{ mW} = V_Z I_Z = (10 \text{ V}) I_Z$$

$$I_Z = 40 \text{ mA}$$

$$I_{s_{\max}} = I_{R_s} - I_{Z_{\max}} = 45.45 \text{ mA} - 40 = 5.45 \text{ mA}$$

$$R_L = \frac{V_L}{I_{s_{\max}}} = 1834.86 \Omega$$

Large R_L reduces I_L & forces more of I_{R_s} to pass thru Zener diode

(d) In absence of Zener diode

$$V_L = 10 \text{ V} = \frac{R_L \times 20}{R_L + 220}$$

$$R_L = 220 \Omega$$